	R/A/G	
Current, potential difference and resistance		
Standard circuit diagram symbols		
-+ cell		
-+ - battery (A) ammeter		
- diode		
thermistor		
variable resistor		
LED		
Electrical charge and current		
For electrical charge to flow through a closed circuit the circuit must include a source		
of potential difference.		
Electric current is a flow of electrical charge.		
The size of the electric current is the rate of flow of electrical charge.		
Charge flow, current and time are linked by the equation: charge flow = current ×time		
Q = I t		
charge flow, Q, in coulombs, C current, I, in amperes, A, time, t, in seconds, s		
A current has the same value at any point in a single closed loop.		
Current, resistance and potential difference		
The current (I) through a component depends on both the resistance (R) of the		
component and the potential difference (V) across the component. The greater the		
resistance of the component the smaller the current for a given potential difference		
(pd) across the component.		
Current, potential difference or resistance can be calculated using the equation:		
potential difference = current ×resistance		
V = I R potential difference, V, in volts, V current, I, in amperes, A, resistance, R, in		
ohms, []		
Use circuit diagrams to set up and check appropriate circuits to investigate the		
factors affecting the resistance of electrical circuits.		
This should include:		
• the length of a wire at constant temperature		
combinations of resistors in series and parallel.		
Kesistors		

For some resistors, the value of R remains constant but that in others it can change as	
the current changes. The current through an ohmic conductor (at a constant	
temperature) is directly proportional to the potential difference across the resistor.	
This means that the resistance remains constant as the current changes.	
The resistance of components such as lamps, diodes, thermistors and LDRs is not	
constant; it changes with the current through the component. The resistance of a	
filament lamp increases as the temperature of the filament increases.	
The current through a diode flows in one direction only.	
The diode has a very high resistance in the reverse direction.	
The resistance of a thermistor decreases as the temperature increases.	
The resistance of an LDR decreases as light intensity increases.	
Required practical activity 16: use circuit diagrams to construct appropriate circuits	
to investigate the I-V characteristics of a variety of circuit elements, including a	
filament lamp, a diode and a resistor at constant temperature.	
Series and parallel circuits	
There are two ways of joining electrical components, in series and in parallel. Some	
circuits include both series and parallel parts.	
For components connected in series:	
 there is the same current through each component 	
• the total potential difference of the power supply is shared between the components	
\cdot the total resistance of two components is the sum of the resistance of each	
component.	
R_{total} = R1 + R2 resistance, R, in ohms, Ω	
For components connected in parallel:	
$m \cdot$ the potential difference across each component is the same	
ullet the total current through the whole circuit is the sum of the currents through the	
separate components	
$m \cdot$ the total resistance of two resistors is less than the resistance of the smallest	
individual resistor.	
Domestic uses and safety	
Direct and alternating potential difference	
Mains electricity is an ac supply. In the United Kingdom the domestic electricity supply	
has a frequency of 50 Hz and is about 230 V.	
Most electrical appliances are connected to the mains using threec ore cable.	
The insulation covering each wire is colour coded for easy identification:	
live wire - brown	
neutral wire - blue	
earth wire - green and yellow stripes. T	
he live wire carries the alternating potential difference from the supply. The neutral	
wire completes the circuit. The earth wire is a safety wire to stop the appliance	
becoming live. The potential difference between the live wire and earth (0 V) is about	

230 V. The neutral wire is at, or close to, earth potential (0 V). The earth wire is at 0
v, it only carries a current if there is a fault.
Energy transfers
Power
Students should be able to explain how the power transfer in any circuit device is
related to the potential difference across it and the current through it, and to the
energy changes over time:
ower = potential difference ×current
P =V I power = current 2 ×resistance P = I2 R power, P, in watts, W potential
difference, V, in volts, V current, I, in amperes, A, resistance, R, in ohms, Ω
Energy transfers in everyday appliances
Everyday electrical appliances are designed to bring about energy transfers. The
amount of energy an appliance transfers depends on how long the appliance is switched
on for and the power of the appliance.
Work is done when charge flows in a circuit. The amount of energy transferred by
electrical work can be calculated using the equation:
energy transferred = power ×time E = P t
energy transferred = charge flow × potential difference
E =Q V
energy transferred, E, in joules, J power, P, in watts, W time, t, in seconds, s charge
flow, Q, in coulombs, C potential difference, V, in volts, V
The National Grid
The National Grid is a system of cables and transformers linking power stations to
consumers.
Electrical power is transferred from power stations to consumers using the National
Grid.
Step-up transformers are used to increase the potential difference from the power
station to the transmission cables then step-down transformers are used to decrease,
to a much lower value, the potential difference for domestic use.

Current and circuit symbols

Define the term current and give the unit.

Define the term voltage and give the unit.

Define the term resistance and give the unit.

Give the equation used to calculate charge:

Match the terms below:



Placed in parallel; measures the potential difference across a component Flow of electric charge Component; resistance decreases as temperature increases Charge/ current moves in one direction around the circuit Voltage; energy transferred per unit of charge Charge/ current changes direction Placed in series; measures the current Component; resistance decreases as intensity of light increases Calculated using the equation V ÷ I

Label the circuit symbols with the correct word:





Resistance and Ohm's Law

Give the equation for Ohm's law and show the rearrangements.

Use the diagram to explain how to investigate the factors affecting resistance:



Draw graphs showing voltage against current for each of the following components and explain what it shows.

Diode



Filament Lamp



Fixed Resistor



Changing Resistance of LDRS and Thermistors

Thermistor

Resistance

Temperature	

Light Dependent Resistor

Resistance

Light Intensity

Series Circuits

Series – Means that all the components are connected in one loop.



Label the diagram with the current at each point

Series Circuit Current Rule:

Current is _____

Because _____

<u>Voltage</u>



Label the diagram with the voltage at each point

Series Circuit Voltage Rule:

Voltage is _____

Because _____

Calculating total resistance in a series circuit:



Parallel Circuits

Parallel - Means that the components are connected in multiple loops.

Current



<u>Voltage</u>



Label the diagram with the voltage at each point

Parallel Circuit Voltage Rule:

Voltage is _____

Because _____

Circuits in the home

Explain the features of a common plug:



Label the graphs to show the difference between A.C. and A.C.





Describe the energy transfers that take place when a kettle boils:



Describe the energy transfers that take place when a fan spins:

Give the two equations for calculating energy transferred:

Give the two equations for calculating power:

The National Grid

What is the National Grid?

Use the diagram below to explain how the National Grid transports electricity to our homes. You should include information to explain the role of step up and step down transformers.



Practice Exam Questions

Q1. The circuit shown has four identical ammeters.



- (a) The table gives the current through two of the ammeters.
 - (i) Complete the table to show the current through the other two ammeters.

Ammeter	Reading on ammeter in amps
A ₁	
A ₂	0.2
A ₃	0.3
A ₄	

(ii) Which **one** of the following statements is correct. Tick (\checkmark) the box next to your choice.

г

٦

The resistance of ${\bf P}$ is more than 20 $\Omega.$	
The resistance of P is equal to 20 Ω .	
The resistance of P is less than 20 Ω .	
Give a reason for your choice.	

(2)

(b)	(i)	Write down the equation that links current, potential difference and resistance.	
			(1)
	(ii)	Calculate the reading on the voltmeter. Show clearly how you work out your answer.	
		Voltmeter reading = volts.	(2)
(iii)	St	ate the potential difference of the power supply.	(2)
			(1)

(c) A second circuit contains an unknown component labelled **X**.



As component \mathbf{X} is heated, the reading on the ammeter goes up.

What is component X?

.....

Give a reason for your answer.

.....

.....

(2) (Total 10 marks)

Q2. A circuit was set up as shown in the diagram.



(a) The table gives the current through three of the ammeters. Complete the table to show the current through the other two ammeters.

Ammeter	Reading on ammeter in amps
A	0.2
A ₂	0.6
A₃	0.3
A,	
A₅	

(b) The reading on the voltmeter is 12 V.

What is the resistance of R_2 ?

Show your working and include the correct unit.

Resistance =

(2)

(c) In the circuit above, the resistor \mathbf{R}_2 burned out and current stopped flowing in it. There was no other change to the circuit. Complete the table below to show the readings on the ammeters after this took place.

Ammeter	Reading on ammeter in amps
A	0.2
A ₂	0.0
A₃	
A₄	
A₅	

(3)

(Total 8 marks)

Q3.An electric current is a flow of electrical charge through a circuit.

(a) Complete the sentence. Use a word from the box.

atoms electrons i	ons molecules
-------------------	---------------

Metals are good conductors of electricity because electrical charge is transferred

by delocalised

(b) Draw **one** line from each symbol to the name of the component.

Standard symbol

Name of component



(1)

(c) The table below shows information about some electrical appliances.

Electrical appliance	Power in watts
Hairdryer	1500
Kettle	2500
Electric hob	3000
Television	360

A student plugs all four of the appliances into one multi-way socket.

The mains electricity is 230 V.

The highest safe current in the socket is 30 A.

Explain why it is not safe to use all four appliances at the same time.

In your answer you should:

- calculate the total power needed
- use the equation

current = power ÷ potential difference

to calculate the total current needed.

(d) The figure below shows how electrical power is transferred from power stations to consumers using the National Grid.

	Transmission cables	
	Power station Transformer 1 Transformer 2 House	
	Transformer 1 is a step-up transformer.	
	Explain why step-up transformers are used in the National Grid.	
		(3)
(e)	What is the purpose of Transformer 2?	
(f)	In a power station 900 MJ of thermal energy were released by burning natural gas.	(1)
	Write down the equation that links efficiency, useful input energy transfer and useful output energy transfer.	
		(1)
(g)	In a power station 900 MJ of thermal energy were released by burning natural gas.	
	Calculate the efficiency of this energy transfer.	
	Efficiency =(2)(Total 15 marks)	

<u>Markscheme</u>

M1.		(a)	(i)	A ₁ = 0.5 ignore any units	1
			A4	= 0.5 allow 1 mark for $A_7 = A_4 \neq 0.5$	1
		(ii)	the	resistance of P is more than 20 Ω	1
			a sr	naller current goes through P / A₂(than 20 Ω) dependent on getting 1ª mark correct accept converse	1
(b)	(i)	pot	tential (difference = current × resistance accept pd / voltage for potential difference accept V = $I \times R$, correct symbols and correct case only accept volts = amps × ohms accept I I R provided subsequent method is correct allow combination of physical quantities and named units allow voltage = $I \times R$	
(ii)	6	(iii)	6	allow 1 mark for correct substitution 2 accept their (b)(ii)	1
	(c) <u>thermistor</u> or				
	£	res	⊢ iistance do i	accept correct circuit symbol allow phonetic spelling <u>e</u> goes down (as temperature of thermistor goes up) not accept changes for goes down	1
			do 1 1	not accept an answer in terms of current only	

M2.		(a)	0.9		1
		1.1		accept the value of A₄ + 0.2	1
	(b)	V =	l R or	$12 = 0.6 \text{ R or } \frac{12}{0.6} = ?$	
				accept V = A R V = I × ohm's sign do not credit Ohm's law triangle	2
		R =	20	correct numerical answer earns both marks	
		ohn	าร		1
(c)	A ₃ =	= 0.3			
		A4 =	0.3	accept the same numeric value as A₃	
		A5 =	0.5	accept the value of A₄ + 0.2	3
МЗ.((a)	elect	rons		
	(b)	-0	»	Lamp LED	

extra lines from a symbol negate the mark

Switch

(c) the total power = 7360 watts
 current = 7360 ÷ 230
 1

[8]

1

3

= 32 A

->*

	allow 32 with no working shown for 3 marks	1
	so the current is greater than 30 A	1
(d)	to increase the voltage (across the cables) or to decrease the current (through the cables)	1
	reducing energy losses (in the cables) do not allow electricity for energy do not allow no energy loss	1
	increasing the efficiency of transmission	1
(e)	to decrease the potential difference for domestic use	1
(f)	efficiency = useful output energy transfer total input energy transfer	
(g)	405 / 900	1
	=0.45 accept 45% allow 0.45 or 45% with no working shown for 2 marks	1 [15]